

# IAA6007: Computer Architecture

## Ch.1. Digital Logic Circuits


Wooil Kim  
Dept. of Computer Science & Engineering  
Incheon National University

2019 Fall

- Digital computers
- Logic gates
- Boolean algebra
- Map simplification
- Combinational circuits
- Flip-flops
- Sequential circuits





# 1-1. Digital computers

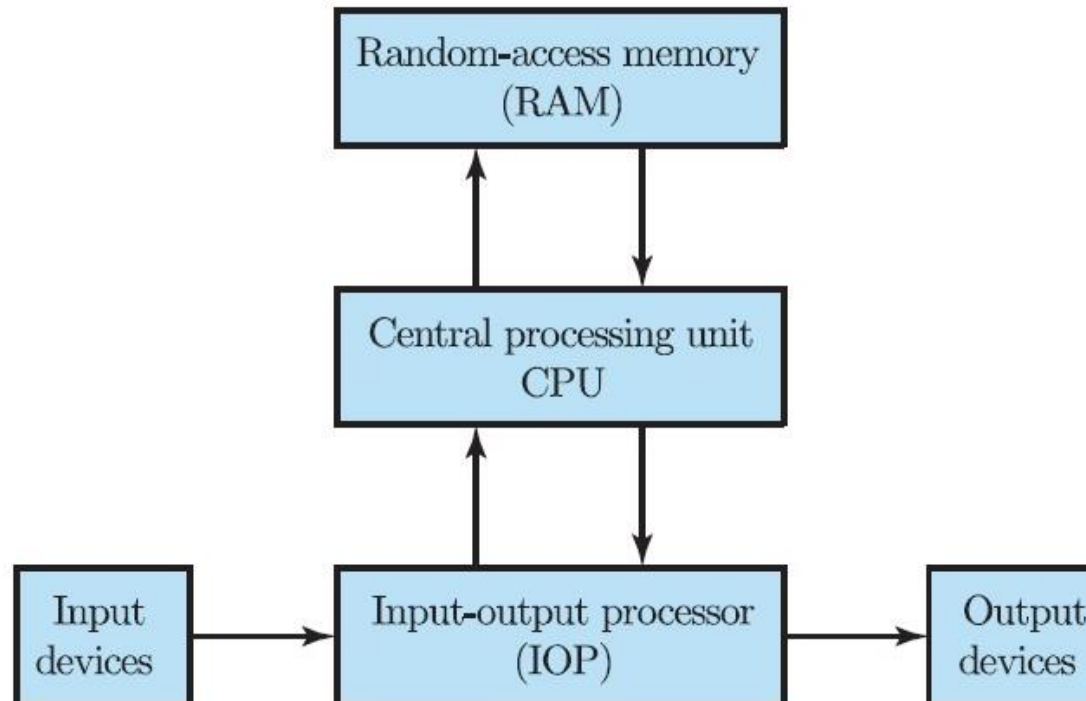- Digital computers use the binary number system, which has two digits 0 and 1
- Groups of bits are used to represent binary numbers, symbols, decimal digits or letters of the alphabet



# 1-2. Logic gates

- Two different voltages represent binary values 0 and 1
  - Ex) a signal of 3 volts represent 1, and 0.5 volt represents 0
- Gates – circuits which perform operation on binary values

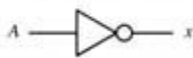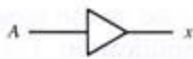Name	Graphic symbol	Algebraic function	Truth table															
AND		$x = A \cdot B$ or $x = AB$	<table><tr><th>A</th><th>B</th><th>x</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	A	B	x	0	0	0	0	1	0	1	0	0	1	1	1
A	B	x																
0	0	0																
0	1	0																
1	0	0																
1	1	1																
OR		$x = A + B$	<table><tr><th>A</th><th>B</th><th>x</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	A	B	x	0	0	0	0	1	1	1	0	1	1	1	1
A	B	x																
0	0	0																
0	1	1																
1	0	1																
1	1	1																
Inverter		$x = A'$	<table><tr><th>A</th><th>x</th></tr><tr><td>0</td><td>1</td></tr><tr><td>1</td><td>0</td></tr></table>	A	x	0	1	1	0									
A	x																	
0	1																	
1	0																	
Buffer		$x = A$	<table><tr><th>A</th><th>x</th></tr><tr><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td></tr></table>	A	x	0	0	1	1									
A	x																	
0	0																	
1	1																	





NAND	 $x = (AB)'$	<table><tr><th>A</th><th>B</th><th>x</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	A	B	x	0	0	1	0	1	1	1	0	1	1	1	0
A	B	x															
0	0	1															
0	1	1															
1	0	1															
1	1	0															
NOR	 $x = (A + B)'$	<table><tr><th>A</th><th>B</th><th>x</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	A	B	x	0	0	1	0	1	0	1	0	0	1	1	0
A	B	x															
0	0	1															
0	1	0															
1	0	0															
1	1	0															
Exclusive-OR (XOR)	 $x = A \oplus B$ or $x = A'B + AB'$	<table><tr><th>A</th><th>B</th><th>x</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	A	B	x	0	0	0	0	1	1	1	0	1	1	1	0
A	B	x															
0	0	0															
0	1	1															
1	0	1															
1	1	0															
Exclusive-NOR or equivalence	 $x = (A \oplus B)'$ or $x = A'B' + AB$	<table><tr><th>A</th><th>B</th><th>x</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	A	B	x	0	0	1	0	1	0	1	0	0	1	1	1
A	B	x															
0	0	1															
0	1	0															
1	0	0															
1	1	1															

Figure 1-2 Digital logic gates.


# 1-3. Boolean algebra

- Boolean function
  - Algebraic expression
  - Ex)  $F = x + y'z$ , where  $x, y, z$  are binary variables
  - A Boolean function may be expressed with a truth table
  - A Boolean function can be transformed from an algebraic expression into a logic diagram

Figure 1-3 Truth table and logic diagram for  $F = x + y'z$ .

$x$	$y$	$z$	$F$
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

(a) Truth table

 

(b) Logic diagram

# 1-3. Boolean algebra

- A Boolean function can be expressed algebraically in many different ways
  - One may obtain a simpler expression that requires fewer gates


**TABLE 1-1** Basic Identities of Boolean Algebra

(1) $x + 0 = x$	(2) $x \cdot 0 = 0$
(3) $x + 1 = 1$	(4) $x \cdot 1 = x$
(5) $x + x = x$	(6) $x \cdot x = x$
(7) $x + x' = 1$	(8) $x \cdot x' = 0$
(9) $x + y = y + x$	(10) $xy = yx$
(11) $x + (y + z) = (x + y) + z$	(12) $x(yz) = (xy)z$
(13) $x(y + z) = xy + xz$	(14) $x + yx = (x + y)(x + z)$
(15) $(x + y)' = x'y'$	(16) $(xy)' = x' + y'$
(17) $(x')' = x$	


# 1-3. Boolean algebra

- DeMorgan's theorem
  - $(x + y + z)' = x'y'z'$ ,  $(xyz)' = x' + y' + z'$

Figure 1-4 Two graphic symbols for NOR gate.

 


(a) OR-invert

 


(b) invert-AND

Figure 1-5 Two graphic symbols for NAND gate.

 


(a) AND-invert

 


(b) invert-OR
 
# 1-3. Boolean algebra

- Ex)  $F = ABC + ABC' + A'C$ 
  - $F = ABC + ABC' + A'C = AB(C + C') + A'C$   
 $= AB + A'C$



(a)  $F = ABC + ABC' + A'C$

 

(B)  $F = AB + A'C$

Figure 1-6 Two logic diagrams for the same Boolean function.



# 1-3. Boolean algebra

- Complement of a function

- Can be derived from DeMorgan's theorem

- Ex)  $F = AB + C'D' + B'D$

- $$\begin{aligned} F' &= (AB + C'D' + B'D)' \\ &= (AB)'(C'D')'(B'D)' \\ &= (A' + B')(C + D)(B + D') \end{aligned}$$

- Also can be obtained by taking duals and complementing each literal

- Interchange OR and AND

- $F = AB + C'D' + B'D$

- $F' = (A' + B')(C + D)(B + D')$

# 1-4. Map simplification

- Minterm: each combination of the variables
  - $x, y \rightarrow xy, x'y, xy', x'y'$
  - $n$  variables  $\rightarrow 2^n$  minterms
- Sum of Products (SOP)
  - Boolean expression ORing AND terms
  - $F = y' + xy + x'y'z'$
- Product of Sums (POS)
  - Boolean expression ANDing OR terms
  - $F = y'(x + y)(x' + y' + z')$

# 1-4. Map simplification

- Canonical SOP form
  - Boolean function expressed as sum of minterms
  - A Boolean function may be converted to a canonical SOP form
  - Ex)  $F(x, y, z) = y' + xy + x'yz'$

$$= y'(x + x') + xy(z + z') + x'yz'$$

$$= xy' + x'y' + xyz + xyz' + x'yz'$$

$$= xy'(z + z') + x'y'(z + z') + xyz + xyz' + x'yz'$$

$$= xy'z + xy'z' + x'y'z + x'y'z' + xyz + xyz' + x'yz'$$

# 1-4. Map simplification

- A Boolean function may be expressed by listing the decimal equivalent of those minterms that produce 1


- Ex)  $F(x, y, z) = xy'z + xy'z' + x'y'z + x'y'z' + xyz + xyz' + x'yz'$   
 $= \Sigma (0, 1, 2, 4, 5, 6, 7)$

- Ex)  $F(x, y, z) = \Sigma (1, 4, 5, 6, 7)$   
 $= x'y'z + xy'z' + xy'z + xyz' + xyz$


$x$	$y$	$z$	$F$
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

# 1-4. Map simplification


- Karnaugh map (K-map)

 

(a) Two-variable map

 

(b) Three-variable map

 


(c) Four-variable map

# 1-4. Map simplification

- Step 1: Insert 1's in those squares where the function is 1
- Step 2: Combine the squares containing 1's in groups of adjacent squares
  - Must contain a number of squares that is an integral power of 2 (e.g., 2, 4, 8, ...)
  - Groups of combined adjacent squares may share one or more
- Step 3: Take OR of those terms
  - Each group of squares represents an algebraic term

# 1-4. Map simplification


- Ex)  $F(A, B, C) = \Sigma(3, 4, 6, 7)$

 

- $F = BC + AC'$
 
# 1-4. Map simplification

- Ex)  $F(A, B, C) = \Sigma(0, 2, 4, 5, 6)$




- $F = C' + AB'$


 
# 1-4. Map simplification


- Ex)  $F(A, B, C, D) = \Sigma(0, 1, 2, 6, 8, 9, 10)$



- $F = B'D' + B'C' + A'CD'$
 
# 1-4. Map simplification

- Product of sums simplification
  - Ex)  $F(A, B, C, D) = \Sigma(0, 1, 2, 5, 8, 9, 10)$
- Sum of products (SOP)
  - $F = B'D' + B'C' + A'C'D$
- Combine squares of 0
  - $F' = AB + CD + BD'$
- Product of Sums (POS)
  - By DeMorgan's theorem
  - $F = (A' + B')(C' + D')(B' + D)$



# 1-4. Map simplification

- Product of sums

Figure 1-12 Logic diagrams with AND and OR gates.

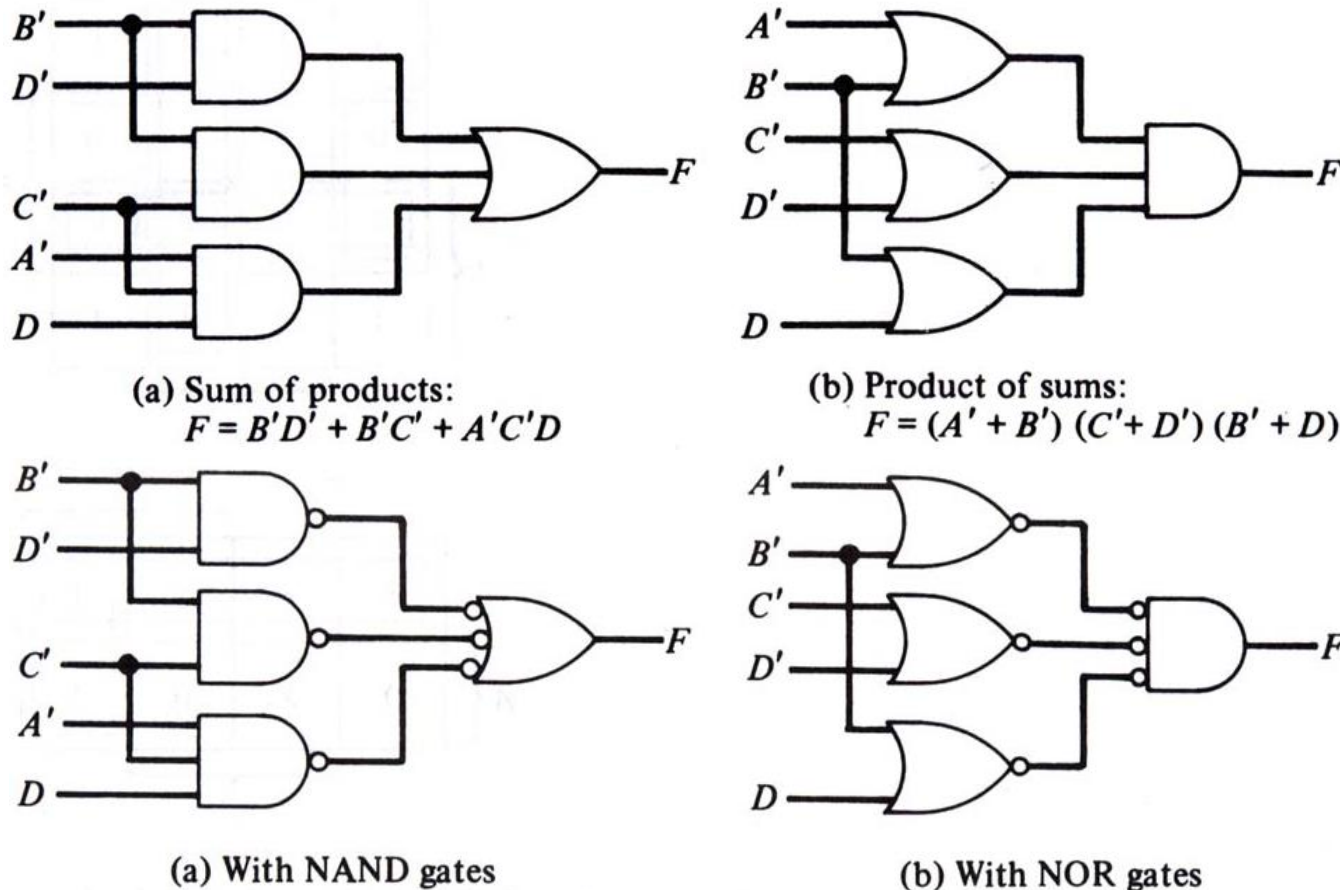


Figure 1-13 Logic diagrams with NAND or NOR gates.


# 1-4. Map simplification

- Don't care conditions
  - Not matter if function produce 0 or 1
- Ex)  $F(A, B, C) = \Sigma(0, 2, 6)$ 
  - $d(A, B, C) = \Sigma(1, 3, 5)$ ; don't care condition
  - $F = A' + BC'$
  - $F = A'C' + BC'$ ; not good

	$B$			
$A$	1	×	×	1
	0	×	0	1
	$C$			
 
# 1-4. Map simplification

- Ex) Simplify the Boolean function,  $F = A'C + A'B + AB'C + BC$




Copyright ©2013 Pearson Education, publishing as Prentice Hall


- $F = C + A'B$
 
# 1-4. Map simplification

- Ex) Simplify the Boolean function
- $F(w, x, y, z) = \Sigma(1, 3, 7, 11, 15)$
- Don't-care conditions,  $d(w, x, y, z) = \Sigma(0, 2, 5)$




(a)  $F = yz + w'x'$

 

(b)  $F = yz + w'z$
 
# 1-5. Combinational circuits

- Connected arrangement of logic gates with a set of inputs and outputs
- Can be described by a truth table
  - Shows binary relationship between  $n$  input variables and  $m$  output variables




# 1-5. Combinational circuits

- Half adder

$x$	$y$	$C$	$S$
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

(a) Truth table

 

(b) Logic diagram


- $S = x'y + xy' = x \oplus y$
- $C = xy$




# 1-5. Combinational circuits

- Full adder

Inputs			Outputs	
$x$	$y$	$z$	$C$	$S$
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

 
 
$$S = x'y'z + x'yz' + xy'z' + xyz$$
$$= x \oplus y \oplus z$$




$$C = xy + xz + yz$$
$$= xy + (x'y + xy')z$$

 
# 1-5. Combinational circuits

- Full adder

- $S = x \oplus y \oplus z$
- $C = xy + (x'y + xy')z = xy + (x \oplus y)z$




(a) Logic diagram

 

(b) Block diagram

# 1-6. Flip-flop

- SR flip-flop

 


(a) Graphic symbol

$S$	$R$	$Q(t + 1)$	
0	0	$Q(t)$	No change
0	1	0	Clear to 0
1	0	1	Set to 1
1	1	?	Indeterminate

(b) Characteristic table

# 1-6. Flip-flop

- D flip-flop

 

(a) Graphic symbol


$D$	$Q(t + 1)$
0	0
1	1

Clear to 0  
Set to 1

(b) Characteristic table

# 1-6. Flip-flop

- JK flip-flop

 


(a) Graphic symbol

$J$	$K$	$Q(t+1)$	
0	0	$Q(t)$	No change
0	1	0	Clear to 0
1	0	1	Set to 1
1	1	$Q'(t)$	Complement

(b) Characteristic table

# 1-6. Flip-flop

- T flip-flop

 



(a) Graphic symbol

$T$	$Q(t+1)$
0	$Q(t)$ No change
1	$Q'(t)$ Complement



(b) Characteristic table
  
# 1-6. Flip-flop

- Edge-triggered flip-flop
  - State change is synchronized during a clock pulse transition



  
(a) Positive-edge-triggered *D* flip-flop.



(b) Negative-edge-triggered *D* flip-flop.

# 1-6. Flip-flop

 
- Example of edge-triggered flip-flop
  - Positive-edge-triggered JK flip-flop
  - Q: Initially set to 1





# 1-6. Flip-flop

 - Example of edge-triggered flip-flop
  - Positive-edge-triggered JK flip-flop
  - Q: Initially set to 1



# 1-6. Flip-flop


- Excitation table

SR flip-flop				D flip-flop		
$Q(t)$	$Q(t + 1)$	$S$	$R$	$Q(t)$	$Q(t + 1)$	$D$
0	0	0	×	0	0	0
0	1	1	0	0	1	1
1	0	0	1	1	0	0
1	1	×	0	1	1	1

JK flip-flop				T flip-flop		
$Q(t)$	$Q(t + 1)$	$J$	$K$	$Q(t)$	$Q(t + 1)$	$T$
0	0	0	×	0	0	0
0	1	1	×	0	1	1
1	0	×	1	1	0	1
1	1	×	0	1	1	0


# 1-7. Sequential circuits

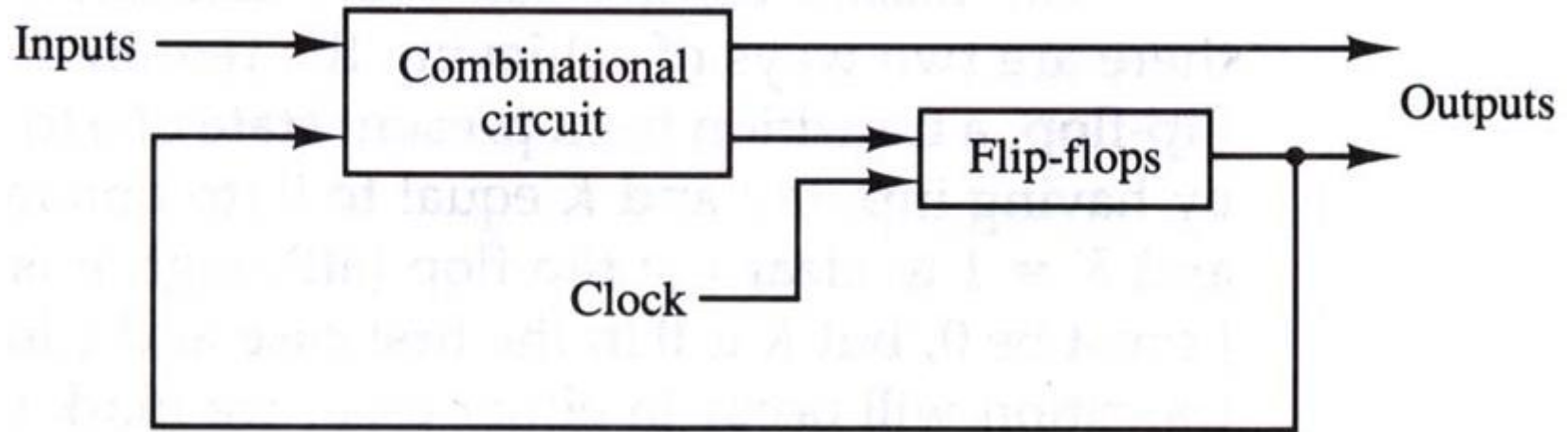

- Analysis
  - Drive Boolean functions for combinational circuits
    - Flip-flops' inputs and outputs
  - Find state table
  - Obtain state diagram

# 1-7. Sequential circuit

- Analysis of sequential circuit

 

# 1-7. Sequential circuit

- Flip-flop input equations
  - $D_A = Ax + Bx, D_B = A'x$
- Combinational circuit output equation
  - $y = Ax' + Bx'$

# 1-7. Sequential circuit

- State table


Present state		Input	Next state		Output
<i>A</i>	<i>B</i>		<i>A</i>	<i>B</i>	
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	1	0
1	0	0	0	0	1
1	0	1	1	0	0
1	1	0	0	0	1
1	1	1	1	0	0

# 1-7. Sequential circuit

- State table


Present state		Input	Next state		Output
A	B		A	B	
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	1	0
1	0	0	0	0	1
1	0	1	1	0	0
1	1	0	0	0	1
1	1	1	1	0	0

- State diagram

 
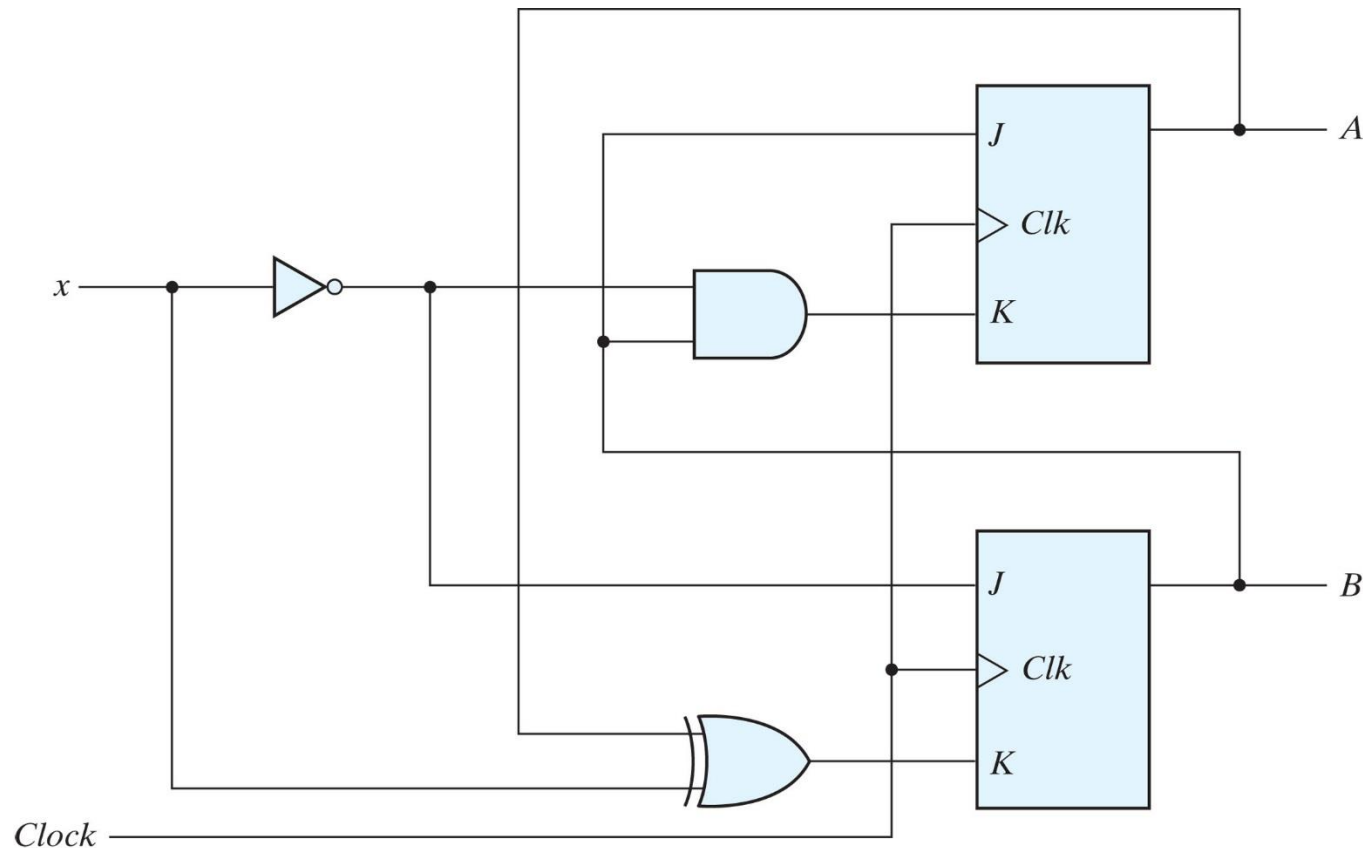
## Ex) Analysis with JK flip-flops

- State equation is not the same as the input equation




Copyright ©2013 Pearson Education, publishing as Prentice Hall


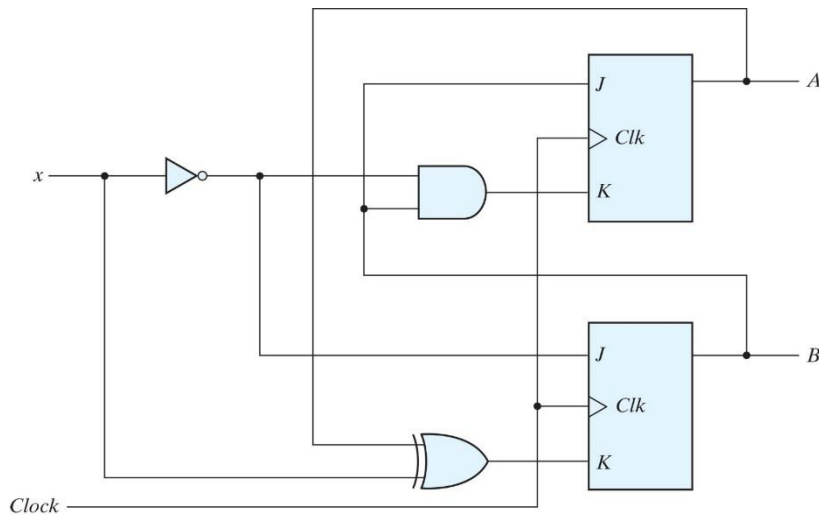
# Analysis with JK flip-flops

- State equation is not the same as the input equation
- Have to refer characteristic table or characteristic equation
- Input equations
  - $J_A = B \quad K_A = Bx'$
  - $J_B = x' \quad K_B = A'x + Ax'$



Copyright © 2013 Pearson Education, publishing as Prentice Hall

# Analysis with JK flip-flops

- State table and state diagram

**Table 5.4**  
*State Table for Sequential Circuit with JK Flip-Flops*

Present State		Input	Next State		Flip-Flop Inputs			
A	B		A	B	$J_A$	$K_A$	$J_B$	$K_B$
0	0	0	0	1	0	0	1	0
0	0	1	0	0	0	0	0	1
0	1	0	1	1	1	1	1	0
0	1	1	1	0	1	0	0	1
1	0	0	1	1	0	0	1	1
1	0	1	1	0	0	0	0	0
1	1	0	0	0	1	1	1	1
1	1	1	1	1	1	0	0	0

Copyright ©2012 Pearson Education, publishing as Prentice Hall


# Analysis with JK flip-flops

- State table and state diagram

**Table 5.4**  
*State Table for Sequential Circuit with JK Flip-Flops*

Present State		Input $x$	Next State		Flip-Flop Inputs			
$A$	$B$		$A$	$B$	$J_A$	$K_A$	$J_B$	$K_B$
0	0	0	0	1	0	0	1	0
0	0	1	0	0	0	0	0	1
0	1	0	1	1	1	1	1	0
0	1	1	1	0	1	0	0	1
1	0	0	1	1	0	0	1	1
1	0	1	1	0	0	0	0	0
1	1	0	0	0	1	1	1	1
1	1	1	1	1	1	0	0	0

 Copyright ©2012 Pearson Education, publishing as Prentice Hall




Copyright ©2013 Pearson Education, publishing as Prentice Hall

# 1-7. Sequential circuit

- Design example
  - Binary counter
- Design procedure
  - (1) translate circuit specification -> (2) state diagram - > (3) state table  
-> (4) logic circuit diagram
- Binary counter
  - Sequence of repeated binary states 00, 01, 10, 11 when external input  $x = 1$
  - State remains unchanged when  $x = 0$
  - Need two flip-flops representing two bits


# 1-7. Sequential circuit

- State diagram

 

# 1-7. Sequential circuit

- State diagram

 

# 1-7. Sequential circuit

- State table

Present state		Input	Next state		Flip-flop inputs			
A	B		A	B	$J_A$	$K_A$	$J_B$	$K_B$
0	0	0	0	0	0	×	0	×
0	0	1	0	1	0	×	1	×
0	1	0	0	1	0	×	×	0
0	1	1	1	0	1	×	×	1
1	0	0	1	0	×	0	0	×
1	0	1	1	1	×	0	1	×
1	1	0	1	1	×	0	×	0
1	1	1	0	0	×	1	×	1

# 1-7. Sequential circuit


- State table

Present state		Input	Next state		Flip-flop inputs			
A	B		A	B	$J_A$	$K_A$	$J_B$	$K_B$
0	0	0	0	0	0	×	0	×
0	0	1	0	1	0	×	1	×
0	1	0	0	1	0	×	×	0
0	1	1	1	0	1	×	×	1
1	0	0	1	0	×	0	0	×
1	0	1	1	1	×	0	1	×
1	1	0	1	1	×	0	×	0
1	1	1	0	0	×	1	×	1




# 1-7. Sequential circuit


- K-maps

 


$$J_A = Bx$$

 

$$K_A = Bx$$

 


$$J_B = x$$

 

$$K_B = x$$


# 1-7. Sequential circuit

- Logic diagram

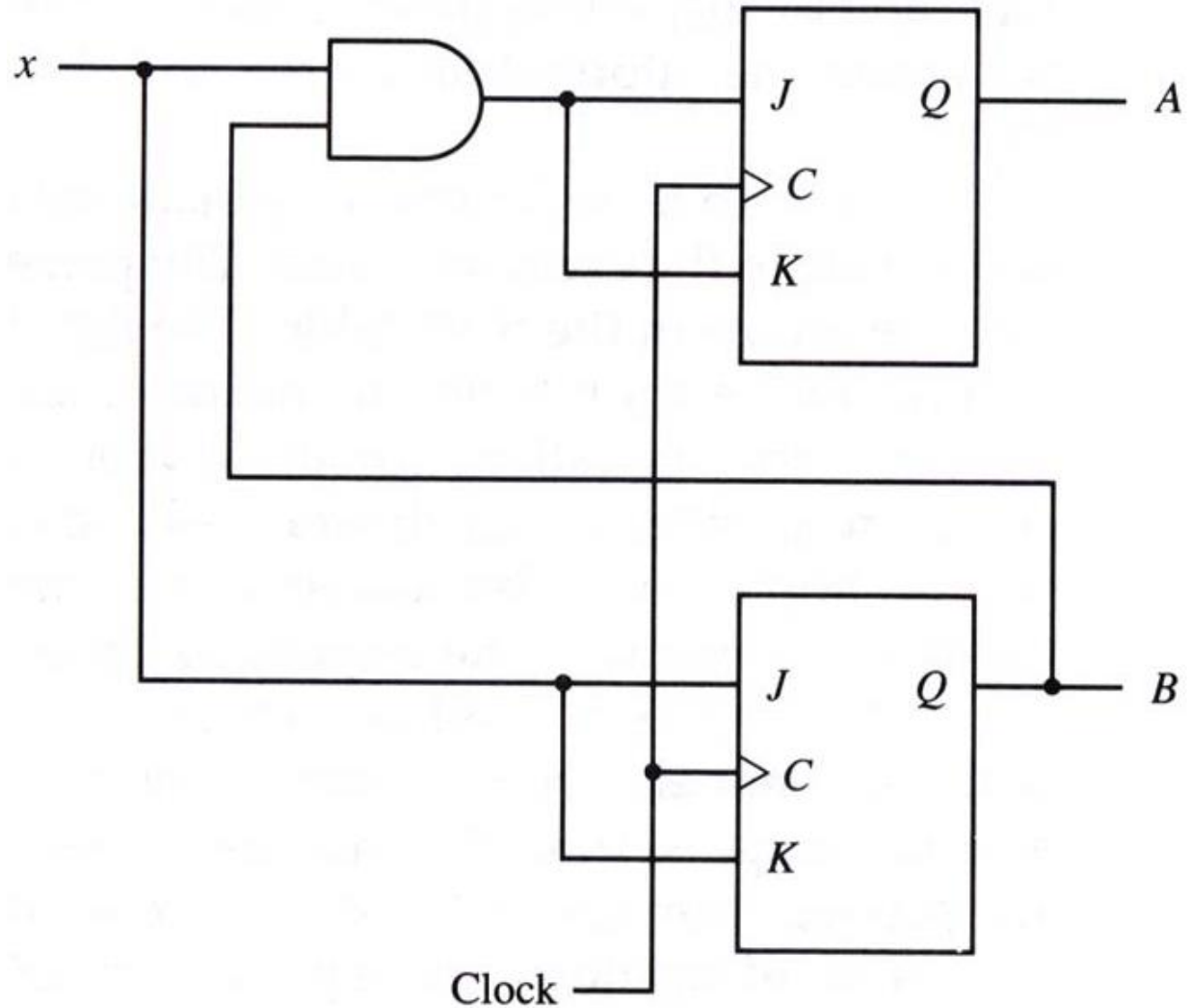
 
# Ex) Synthesis using T flip-flops


- 3-bit binary counter
  - 3-bit counter has 3 flip-flops and can count from 0 to  $2^n-1$  ( $n=3$ )



Copyright ©2013 Pearson Education, publishing as Prentice Hall
 
# Synthesis using T flip-flops


- 3-bit binary counter
  - 3-bit counter has 3 flip-flops and can count from 0 to  $2^n - 1$  ( $n=3$ )



Copyright ©2013 Pearson Education, publishing as Prentice Hall
 
# Synthesis using T flip-flops

- 3-bit binary counter
  - 3-bit counter has 3 flip-flops and can count from 0 to  $2^n-1$  ( $n=3$ )



Copyright ©2012 Pearson Education, publishing as Prentice Hall

**Table 5.14**  
*State Table for Three-Bit Counter*

Present State			Next State			Flip-Flop Inputs		
$A_2$	$A_1$	$A_0$	$A_2$	$A_1$	$A_0$	$T_{A2}$	$T_{A1}$	$T_{A0}$
0	0	0	0	0	1	0	0	1
0	0	1	0	1	0	0	1	1
0	1	0	0	1	1	0	0	1
0	1	1	1	0	0	1	1	1
1	0	0	1	0	1	0	0	1
1	0	1	1	1	0	0	1	1
1	1	0	1	1	1	0	1	1
1	1	1	0	0	0	1	1	1

Copyright ©2012 Pearson Education, publishing as Prentice Hall

# Synthesis using T flip-flops

- State table

**Table 5.14**  
*State Table for Three-Bit Counter*

Present State			Next State			Flip-Flop Inputs		
$A_2$	$A_1$	$A_0$	$A_2$	$A_1$	$A_0$	$T_{A2}$	$T_{A1}$	$T_{A0}$
0	0	0	0	0	1	0	0	1
0	0	1	0	1	0	0	1	1
0	1	0	0	1	1	0	0	1
0	1	1	1	0	0	1	1	1
1	0	0	1	0	1	0	0	1
1	0	1	1	1	0	0	1	1
1	1	0	1	1	1	0	1	1
1	1	1	0	0	0	1	1	1

Copyright ©2012 Pearson Education, publishing as Prentice Hall

# Synthesis using T flip-flops

- K-maps

$A_1A_0$		$A_1$			
		00	01	11	10
$A_2$	0	$m_0$	$m_1$	$m_3$ 1	$m_2$
	1	$m_4$	$m_5$	$m_7$ 1	$m_6$

$A_0$

$$T_{A2} = A_1A_0$$

$A_1A_0$		$A_1$			
		00	01	11	10
$A_2$	0	$m_0$	1	1	$m_2$
	1	$m_4$	1	1	$m_6$

$A_0$

$$T_{A1} = A_0$$

$A_1A_0$		$A_1$			
		00	01	11	10
$A_2$	0	1	1	1	1
	1	1	1	1	1


$x$

$$T_{A0} = 1$$

Copyright ©2013 Pearson Education, publishing as Prentice Hall

# Synthesis using T flip-flops

- Logic diagram

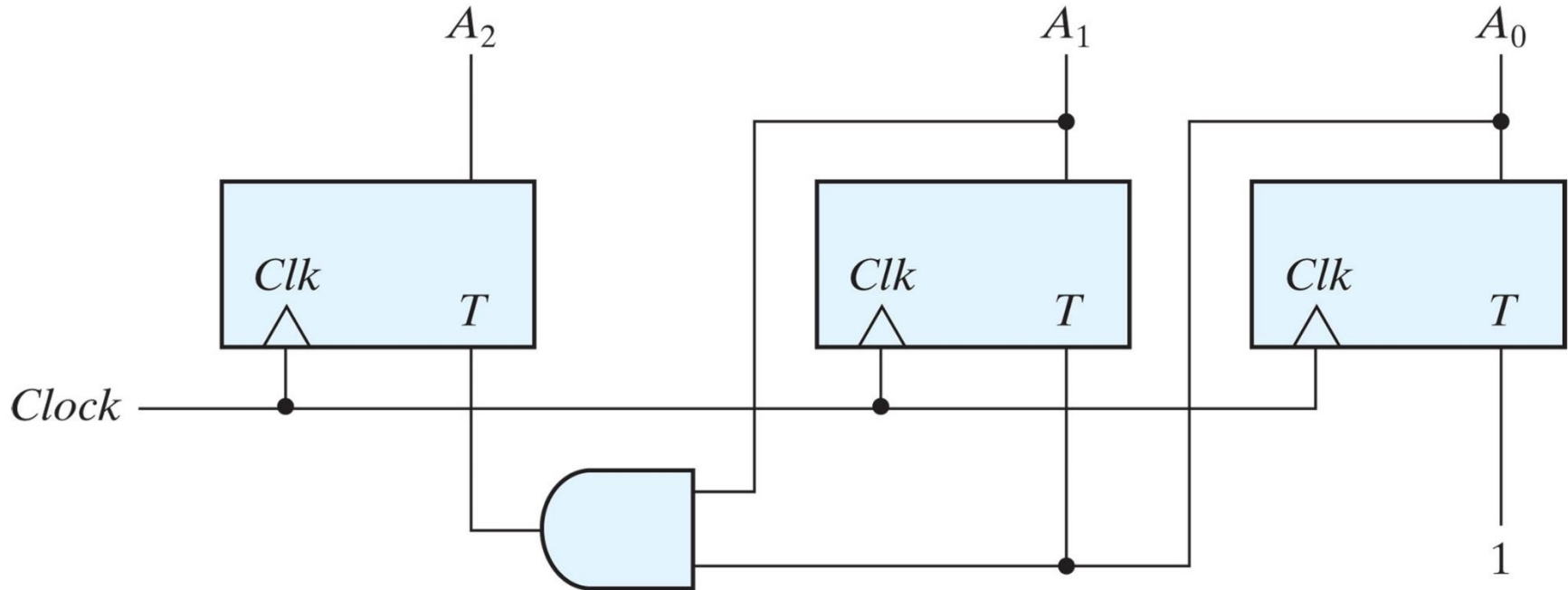

Copyright ©2013 Pearson Education, publishing as Prentice Hall



- 1-2, 1-4, 1-7, 1-8 a, b, 1-9 a, b
- 1-10 a, 1-13, 1-16, 1-19, 1-20